



UNIVERSITY
OF
JOHANNESBURG

PROGRAM : NATIONAL DIPLOMA
ENGINEERING : MECHANICAL

SUBJECT : ELECTROTECHNOLOGY III

CODE : ELT 312

DATE : SUMMER EXAMINATION 2015
9 NOVEMBER 2015

DURATION : (SESSION 1) 08:30 - 11:30

WEIGHT : 40 :60

FULL MARKS : 100

TOTAL MARKS : 100

EXAMINER : MR A.F. COTTRELL 80825003

MODERATOR : MS. C. MAMPANE 2043

NUMBER OF PAGES : 4 PAGES

INSTRUCTIONS : CALCULATORS ARE PERMITTED (ONLY ONE PER STUDENT)

REQUIREMENTS : NONE.

INSTRUCTIONS TO STUDENTS:

1. ANSWER ALL QUESTIONS.
2. RULE OFF AFTER EVERY QUESTION OR SUB-QUESTION.
3. DO NOT ANSWER A QUESTION OR PART THEREOF TWICE. CROSS OUT WHAT YOU DO NOT WANT MARKED.

QUESTION 1

- 1.1 Derive the torque equation of a D.C. machine. (7)
- 1.2 Sketch the torque curves for both the shunt & series motors, explaining the curve shapes. (8)
- 1.3 A shunt machine has armature and field resistances of $0,12 \Omega$ and 120Ω respectively. When connected to a 450 V d.c. supply and driven as a generator at 940 rev/min, it delivers 200 kW. Calculate its speed when running as a motor and taking 50 kW from the same supply. (16)

[31]

QUESTION 2

- 2.1 The following data were obtained during tests on a 150kVA, 1100/420V single phase transformer:

Open Circuit Test	1.1 kV	3.1 A	745 W
Short Circuit Test	40V	110A	880 W (measured on the HV side)

If a given load has a power factor of 0.8, lagging, calculate:

- 3.1.1 Efficiency at full load (6)
 - 3.1.2 I^2R losses at half load (2)
 - 3.1.3 The load kVA at which maximum efficiency will occur .
Is this result reasonable in your opinion? Explain. (2)
 - 3.1.4 The magnetizing current (4)
 - 3.1.5 The equivalent series resistance referred to the LV-side (5)
 - 3.1.6 The equivalent series reactance referred to the HV-side (2)
- 2.2 Draw the full equivalent circuit of a single-phase transformer, including all the voltages and currents. (9)

[30]

QUESTION 3

- 3.1 In Annexure A, Figure 1(a) shows one cycle of three phase currents, marked at points A, B, C, and D.
Figure 1 (b) illustrates four cross-sections of the Stator and Rotor of the same 3-phase, two – pole, induction motor. The beginning of each winding is marked “Red”, “Yellow” & “Blue”, respectively. Fill in the currents flowing, and the flux lines due to the said currents, and thus, show how three phase currents produce a rotating magnetic field, in a 3-phase induction motor. (8)
- 3.2 The power **input** to a 4-pole, 400-volt, 50Hz, 3-phase induction motor is **55** kW. The stator losses total 1.2 kW. If the full load slip is 2.6% , sketch the power flow diagram, and calculate: (7)
- 3.2.1 the Gross mechanical power developed (4)
- 3.2.2 the full load output torque at the shaft, if the mechanical losses amount to 700 watt. (6)
- 3.3 The e.m.f. measured between slip rings on the star connected rotor of a 3-phase, slip ring induction motor is 110 V at standstill. The rotor impedance at standstill, is $(0,2 + j0,55) \Omega/\text{phase}$ and the full load slip is 4%
Calculate at full load:
- 3.3.1 the rotor current. (3)
- 3.3.2 the rotor power factor (2)

[30]

QUESTION 4

- 4.1 A three-phase, star-connected, 2200-volt, 50 Hz alternator has a synchronous impedance of $(1 + j5) \Omega/\text{phase}$. If it has an output of 180 kVA at a power factor of 0.8 lagging, calculate the e.m.f. and load angle. Sketch the phasor diagram for this condition.

[9]

TOTAL

[100]

ANNEXURE A (TO BE HANDED IN, WITH ANSWER BOOK)

NAME: _____

STUDENT NUMBER: _____

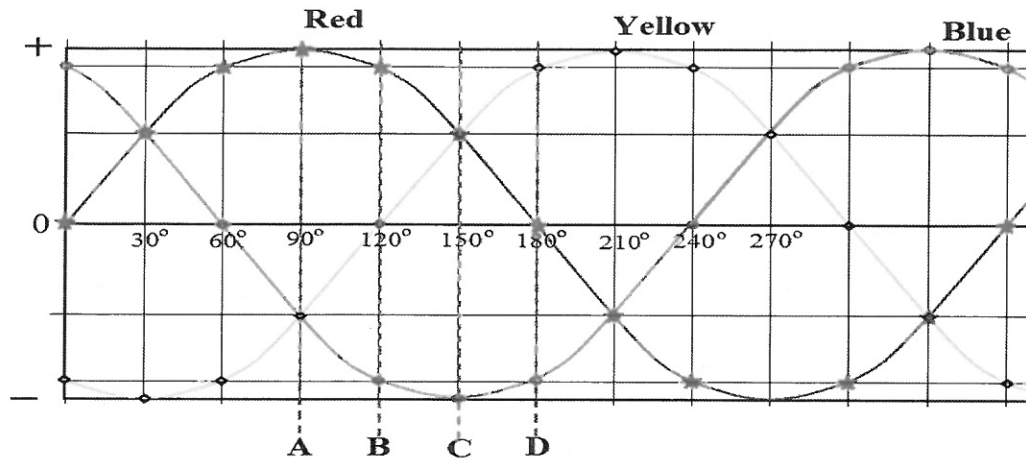


Figure 1 (b)
Three phase currents

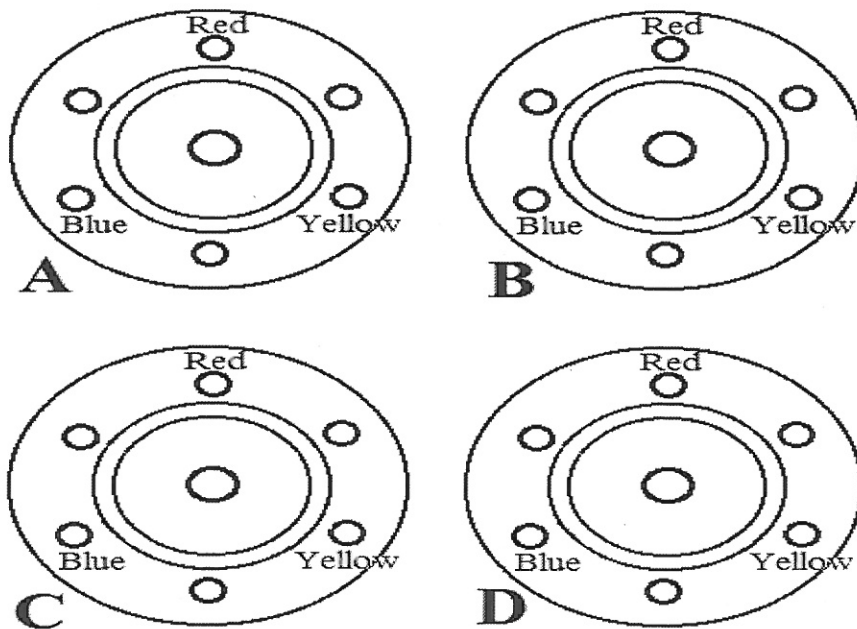


Figure 1 (a)
Cross sectional view of
a three-phase, two-pole
induction motor.