



PROGRAM : NATIONAL DIPLOMA
ENGINEERING : COMPUTER SYSTEMS
ENGINEERING : ELECTRICAL

SUBJECT : **ELECTRICAL ENGINEERING 1**
ELECTROTECHNOLOGY 1

CODE : **AEI1221 / ELT1111**
DATE : WINTER EXAMINATION 2014
19 JUNE 2013

DURATION : (SESSION 2) 12:30 - 15:30

WEIGHT : 40 : 60

TOTAL MARKS : 101

ASSESSOR : MR PR WILSON

MODERATOR : DR DE JAGER

2014

NUMBER OF PAGES : 5 PAGES

INSTRUCTIONS


1. ANSWER ALL QUESTIONS
 2. 1 MARK = 1%
 3. CALCULATORS ARE PERMITTED
-

QUESTION 1


An electric geyser is required to heat 150 litres of water from 22°C to 60°C. The geyser has a 2kw element and an overall efficiency of 85%. If the cost of electricity is R1.15 per kwh determine the cost involved and the time taken to heat the water. Note. The specific heat capacity of water is 4190 J/kg

[8]**QUESTION 2**

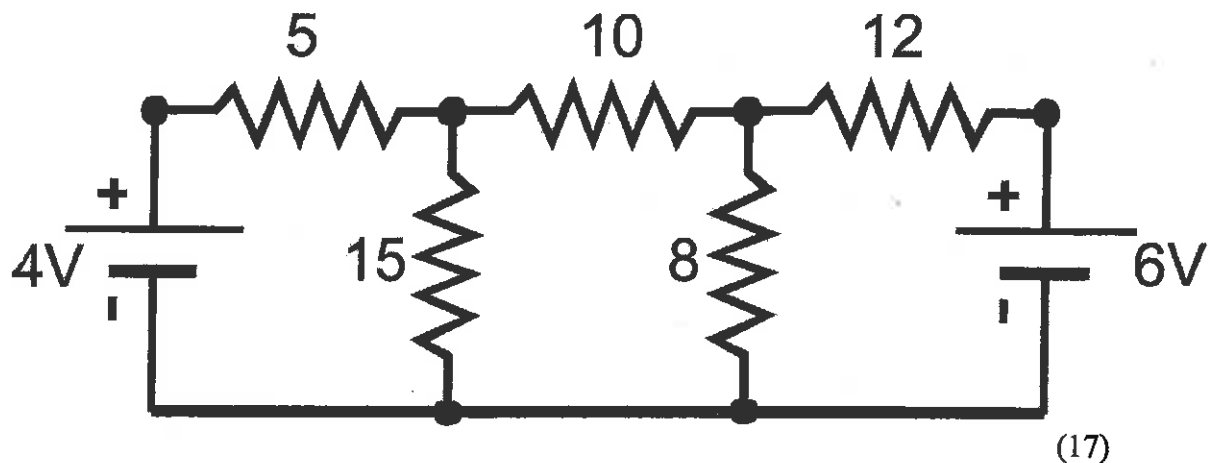
- 2.1 Using the superposition theorem determine the current through the 8Ω resistor.



- 2.2 By conducting a Star to Delta transformation on Star ABC calculate the total current.

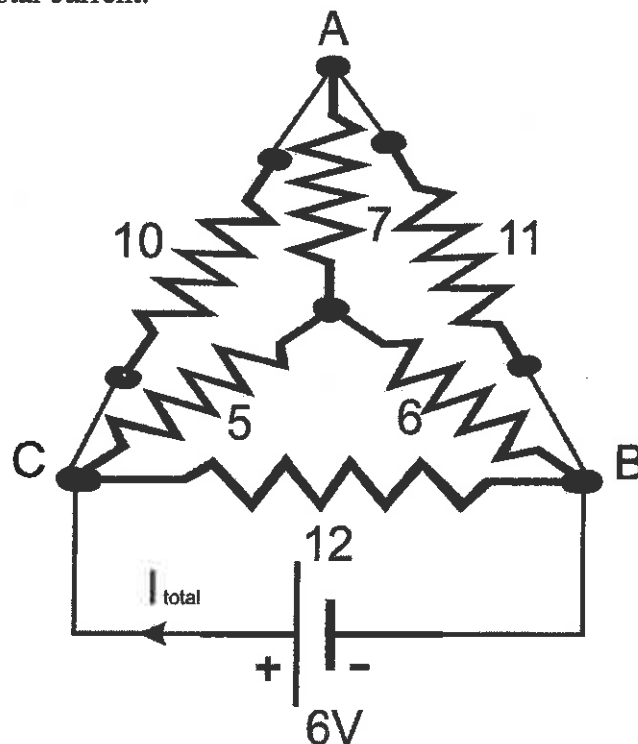**(11)**

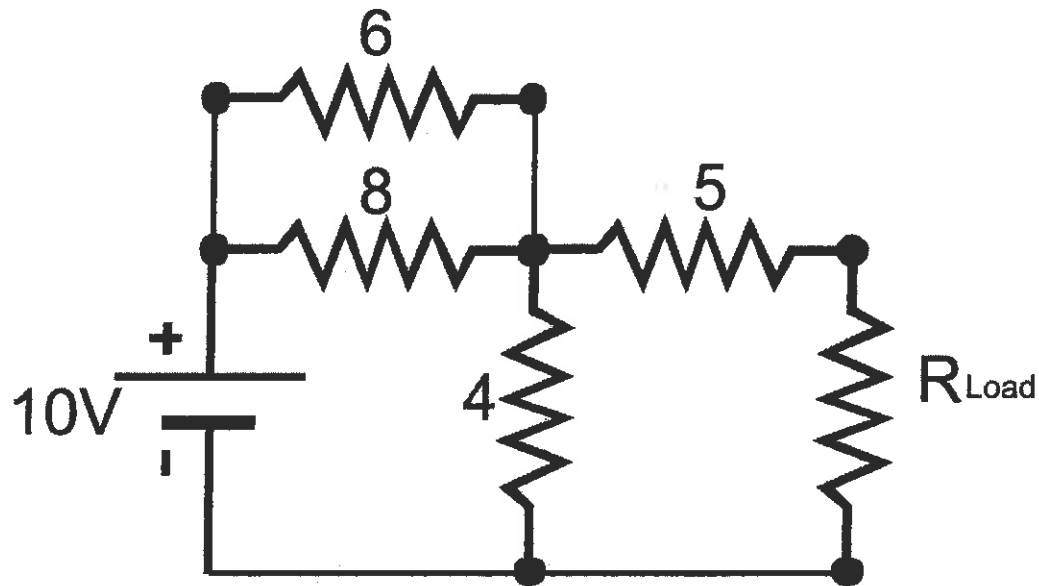2.3 Determine the Thevenin and Norton equivalent of the circuit below.




(10)

[38]

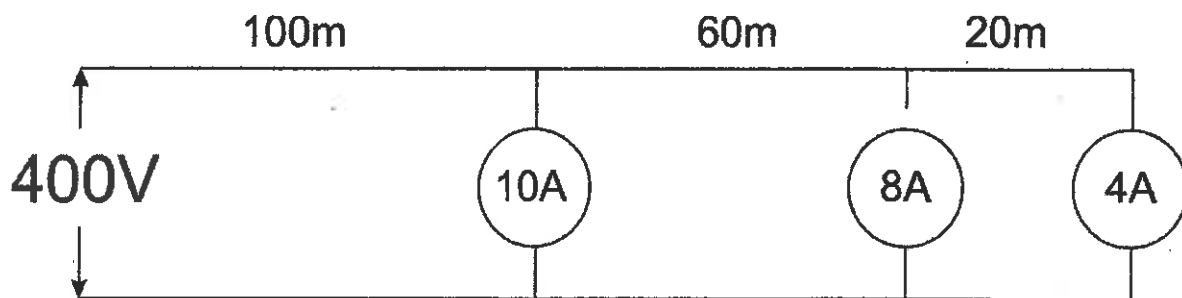QUESTION 3


Calculate the efficiency of the D.C. distribution system if the copper has a diameter of 1.25mm and ρ of $0.017\mu\Omega\text{m}$.




[16]

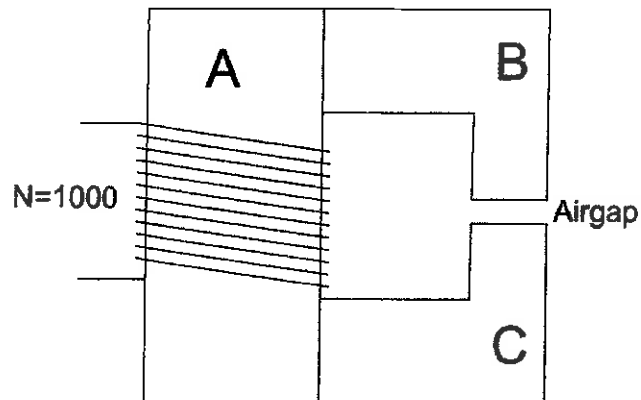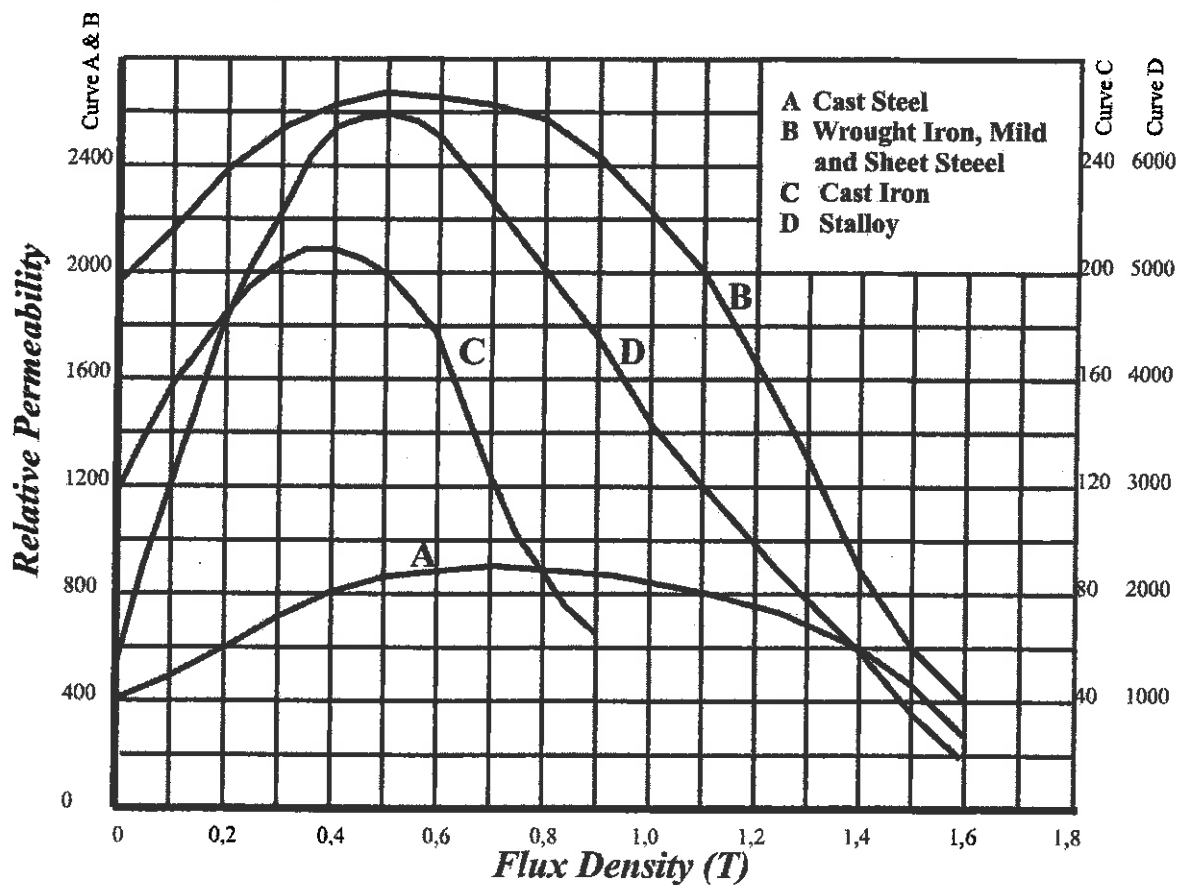QUESTION 4

Calculate the current required to setup a flux density of 0.8 Tesla in the airgap.




Section	Length	Area	Material
A	100mm	80mm ²	Cast Steel
B	50mm	40mm ²	Stalloy
C	50mm	40mm ²	Stalloy
Airgap	1mm	40mm ²	

**[16]**


QUESTION 5

A coil of 1000 turns is wound on a wooden toroidal former. The mean sectional area and length of the magnetic circuit is 20cm^2 and 100mm respectively. The current in the inductor is has the wave form as shown below. Determine and plot the graph of the induced voltage.

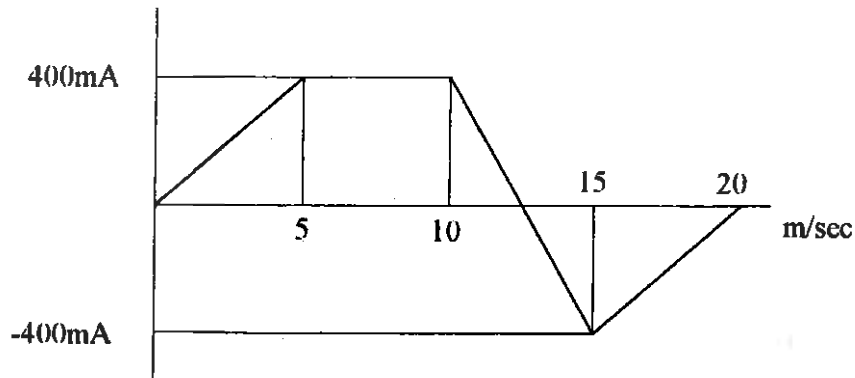**[12]****QUESTION 6**

If $V_{AB} = 10.96\text{V}$ determine the following:

- 6.1 The capacitance of the parallel section AB.
- 6.2 The voltage V_{BC} .
- 6.3 The energy stored in the circuit.

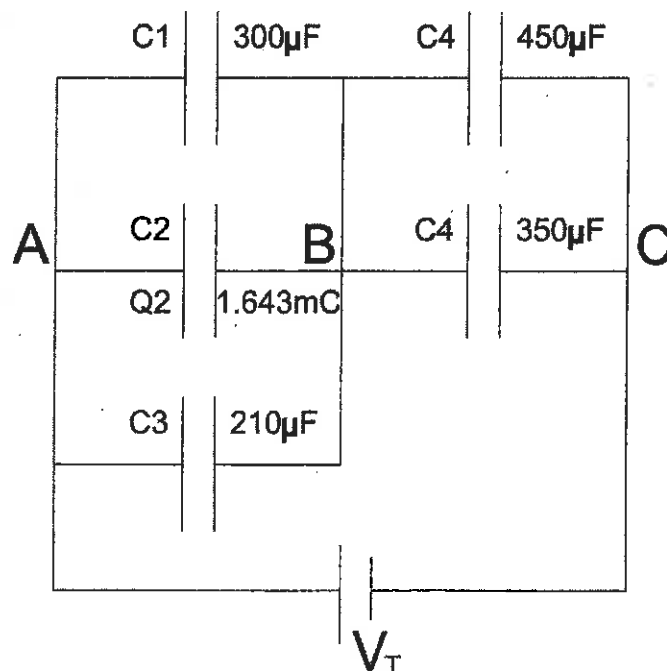**[10]**

Total 100 marks